

Total No. of Questions – [08]

Total No. of Printed Pages [02]

G.R. No.	
----------	--

Paper code - U218-145 (BE-FS)

**MAY 2019/ENDSEM**

**S. Y. B. TECH. (INFORMATION TECHNOLOGY) (SEMESTER - I)**

**COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN**

**COURSE CODE: ITUA21175**

**(PATTERN 2017)**

Time: [2 Hours]

[Max. Marks: 50]

**(\*) Instructions to candidates:**

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q.1) a) Do the following conversions:

[6 marks]

- i)  $(CD6)_{16} = (-----)_{10}$
- ii)  $(1234)_{10} = (-----)_8$
- iii)  $(25.675)_8 = ( )_{16}$

**OR**

- b) Compare Sign Magnitude, 1's Complement, and 2's Complement signed number representations. Give example each and represent  $(-9)_{10}$  using all these representations. [6 marks]

Q.2) a) Explain 3:8 Decoder IC 74138. Design (Truth Table, Logic Function, Circuit Diagram) Full Subtractor using IC 74138. [6 marks]

**OR**

- b) List rules of BCD addition with example. Design (Truth Table, K-map, Logic Function, Circuit Diagram) BCD Adder using IC 7483. [6 marks]

Q.3) a) Draw & Explain 4 bit ring counter with state diagram.

[6 marks]

**OR**

- b) Draw and explain block schematic of IC 7490. Design & draw Mod-5 ( 0 to 5 ) truncated UP counter using IC 74191. [6 marks]

- Q.4) a) Implement the following functions using PLA [4 marks]  
 $A(P, Q, R) = \sum m(0, 2, 4, 6)$   
 $B(P, Q, R) = \sum m(1, 3, 5, 7)$

**OR**

- b) List, draw and explain ASM chart notations. [4 marks]

- Q.5) a) Compare: [6 marks]  
i) Variable and Signals in VHDL.  
ii) Sequential and Concurrent VHDL statements.

- b) Explain the structure of VHDL code with neat diagram. [4 marks]

- c) Declare entity for Full adder and Half adder VHDL modules. [4 marks]

**OR**

- Q.6) a) Declare entity and architecture for 3:8 Decoder VHDL module. [6 marks]

- b) List any 4 operators used in VHDL code and explain each with example. [4 marks]

- c) List the different VHDL program modeling styles and Explain any two of them. [4 marks]

- Q.7) a) Explain 8086 programmer model with neat diagram. [6 marks]

- b) Compare Microprocessor and Microcontroller with their applications. [4 marks]

- c) Draw and explain the Harvard architecture. [4 marks]

**OR**

- Q.8) a) Draw 8086 architecture and explain each functional block. [6 marks]

- b) List applications of Microcontroller and explain any two. [4 marks]

- c) List main features of 8086 Microprocessor. [4 marks]