

Total No. of Questions – [08]

Total No. of Printed Pages: [02]

G.R. No.	
----------	--

paper code: U228-134 (RE-FF)

May 2019/ENDSEM REEXAM

S. Y. B. TECH. (E & TC) (SEMESTER - II)

COURSE NAME: Integrated Circuits (IC)

COURSE CODE: ETUA22174

(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q1 a) Draw neat block diagram of op-amp and describe each block in detail. [6]

OR

b) The following specifications are given for dual input balanced output differential amplifier at room temperature : $I_E = 2.25$ mA, $R_c = 520$ ohms, $\beta_{ac} = \beta_{dc} = 100$, Determine i) Differential voltage gain ii) input resistance and iii) output resistance [6]

Q2 a) Draw the circuit diagram of three op-amp instrumentation amplifier and derive the expression for the gain. [6]

OR

b) For practical integrator the component values are $R_1 = 120$ K ohm, $R_f = 1.2$ M ohm and capacitor $C_f = 10$ nano-farad. [6]
1. draw the circuit diagram
2. determine the integration frequency, f_b
3. Determine the dc gain

Q3 a) What is Schmitt trigger? Draw circuit of inverting Schmitt trigger and describe its working with waveforms. [6]

OR

b) Draw the circuit for inverting comparator. Draw the input and output waveforms with $V_{ref} = -1$ V and $V_{in} = 4\sin(2\pi 100t)$. Draw the transfer characteristics. [6]

Q4 a) Draw circuit diagram of first order butterworth low pass filter and describe its frequency response with the help of gain [4]

equation.

OR

- b) Determine the cut off frequency of second order Butterworth high pass filter if $R = 1 \text{ k ohm}$ and $C = 0.1 \text{ micro farad}$. Determine the gain of circuit at 1.59 KHz and 1 KHz . [4]

- Q5 a) Draw the circuit diagram of $R - 2R$ ladder type DAC. Describe how the circuit converts the code $(1 \ 1)_2$ to $3/4$ volts. Also draw the transfer characteristics [6]
- b) What is the resolution of D to A converter? An 8 bit DAC has reference voltage/ full scale voltage 2.55 V . Determine its resolution/step size. [4]
- c) Draw the circuit diagram of grounded load V to I converter and describe its operation. [4]

OR

- Q6 a) Draw the schematic diagram of 3 bit Successive Approximation (SAR) type ADC. Describe how the circuit works and explain how it gives binary code $(1 \ 0 \ 1)_2$ for analog input 5.2 V . Consider analog input range between 0 to 8 V . [6]
- b) Draw the circuit diagram of high sensitivity I to V converter and describe its operation. [4]
- c) In a 3 bit A to D converter which accepts input voltage between 0 to 2 V , determine output voltage equivalent to 1 LSB/resolution. V_{ref} /Full scale voltage is 2 V . What is the code that the ADC will produce for the input voltage 1.5 ? [4]
- Q7 a) Describe the working of PLL with respect to the block diagram. State any three applications of PLL. [6]
- b) In PLL IC 565 determine free running frequency, lock range and capture range. Given demodulation capacitor $C = 1 \text{ micro Farad}$, Resistor and capacitor of VCO, $R_1 = 15 \text{ k ohms}$ and $C_1 = 0.01 \text{ micro farad}$. $V_{cc} = 12 \text{ V}$ and $-V_{cc} = 0 \text{ V (gnd)}$. [4]
- c) Give any two parameters of PLL and describe them with respect to transfer characteristics of PLL. [4]

OR

- Q8 a) Draw the transfer characteristics of PLL and describe its working with its different modes of operation. [6]
- b) Describe how PLL is used as frequency multiplier? [4]
- c) In PLL IC 565 determine free running frequency, lock range and capture range. Given demodulation capacitor $C = 2 \text{ micro Farad}$, Resistor and capacitor of VCO, $R_1 = 12 \text{ k ohms}$ and $C_1 = 250 \text{ pico farad}$. $V_{cc} = 6 \text{ V}$ and $-V_{cc} = -6 \text{ V}$. [4]