

Total No. of Questions – [03]

Total No. of Printed Pages: 01  
Paper code U239-141 (T1) IT.  
U239-121 (T1) comp.

G.R. No.	
----------	--

**OCTOBER 2019/ INSEM (T1)**  
**S. Y. B.TECH. (COMPUTER ENGINEERING/INFORMATION TECHNOLOGY)**  
**(SEMESTER – III)**  
**COURSE NAME: ANALOG AND DIGITAL ELECTRONICS**  
**COURSE CODE: CSUA21181/ITUA21181**  
**(PATTERN 2018)**  
**(Model Answer)**

Time: [1 Hour]

[Max. Marks: 20]

- Q 1 a) Definition of 1's & 2's complement should be written with one example each [4 marks].  
Map the given SOP expression into K-map and do the grouping of cells [2 marks]  
Obtain minimized expression and design logical circuit diagram [2 marks]
- Q 1 b) Draw minimized table (expected 3 tables) [2 marks]  
Find minimized expression [1 mark]  
Find PI and EPI from the table [1 mark]
- Q 2 a) Design Truth Table for conversion [2 marks]  
Obtain SOP expression [2 marks]  
Map SOP expression into K-Map [2 marks]  
Draw Logical Circuit Diagram [2 marks]
- Q.2 b) Draw block diagram of BCD adder with explanation [2 marks]  
Describe three cases with examples [6 marks]
- Q. 3 a) Draw J-K Flip-Flops block diagram [1 mark]  
Truth Table [1.5 marks]  
Excitation Table [1.5 marks]
- Q.3 b) Draw Truth Table of S-R flip flop [2 marks]  
Draw block diagram for conversion of S-R Flip Flop to J-K Flip Flop [2 marks]