

paper code: U239-133(T1)

OCTOBER/ 2019 INSEM (T1)



S. Y. B.TECH. (E and TC) (SEMESTER – III)


COURSE NAME: Engineering Circuit Analysis

COURSE CODE: ETUA21183 (PATTERN 2018)

SOLUTION & MARKING SCHEME

[Max. Marks: 20]

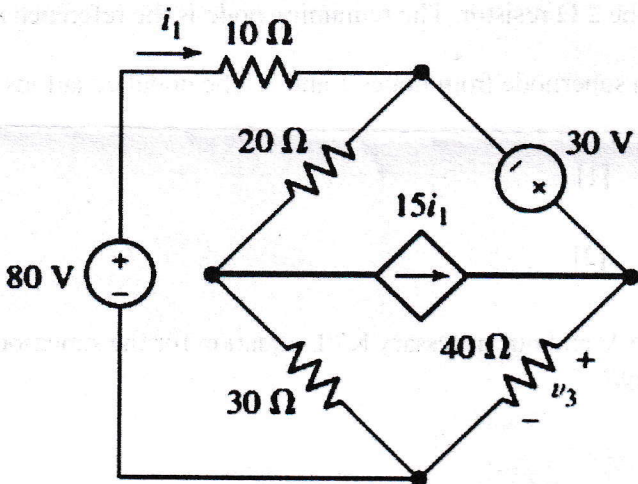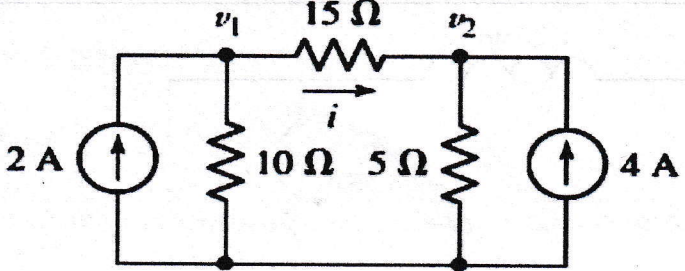Q1	Attempt any ONE [4+4=8M]	CO	BT level
	<p>Determine V_3 that is, voltage across 40 ohm resistor using loop analysis.</p>  <p>Ans: Loop equations – 3M $V_3 = 104.2 \text{ V}$ ----- 1M</p>	CO1	Analysis
	 <p>Node analysis 3 M $V_1 = 20\text{V}$ and $V_2 = 20\text{V}$ Hence current is 0 A ----- 1M</p>	CO1	Analysis
	<p>OR</p> <p>Refer the network below. Using nodal analysis determine all four nodal voltages.</p>	CO1	Analysis

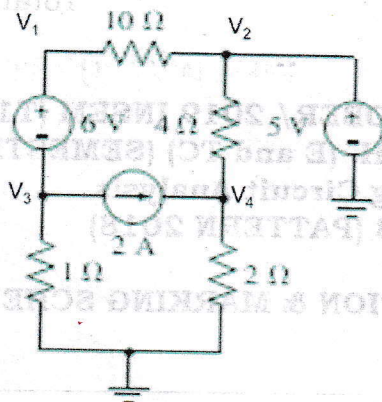

Each node – 1M

We define v_1 at the top left node; v_2 at the top right node; v_3 the top of the 1Ω resistor and v_4 at the top of the 2Ω resistor. The remaining node is the reference node.


We may now form a supernode from nodes 1 and 3. The nodal equations are:

$$-2 = \frac{v_3}{1} + \frac{v_1 - v_2}{10} \quad [1]$$

$$2 = \frac{v_4}{2} + \frac{v_4 - v_2}{4} \quad [2]$$

By inspection, $v_2 = 5\text{ V}$ and our necessary KVL equation for the supernode is $v_1 - v_3 = 6$. Solving,
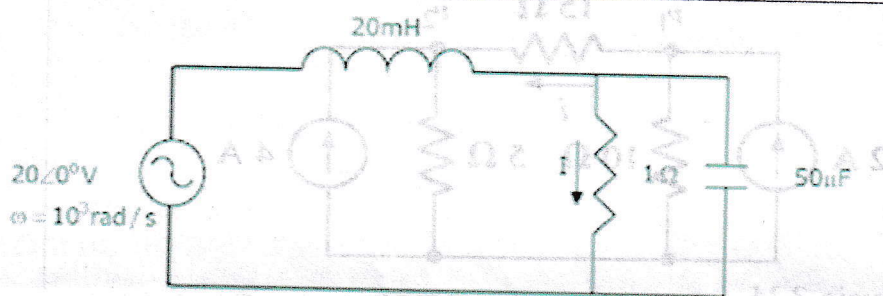
$$\begin{aligned} v_1 &= 4.019\text{ V} \\ v_2 &= 5\text{ V} \\ v_3 &= -1.909\text{ V} \\ v_4 &= 4.333\text{ V} \end{aligned}$$





Conversion into reactances – $20j$ and $-20j$ ----- 1.5 M

Source transformation step- current source- $-j1\text{ A}$ ----- 1.5 M

Answer $I = 1\angle -90^\circ\text{ A} = -j\text{ A}$ ----- 1 M

Q2 | Attempt any ONE [4+4=8M]

CO1 Analysis

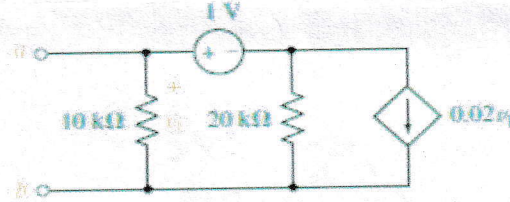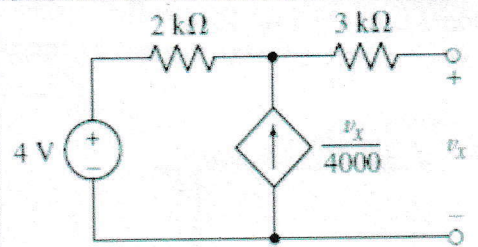	<p>(a) With the right-hand voltage source short-circuited and the current source open-circuited, we have $2 \parallel 5 = 10/7 \Omega$</p> <p>By voltage division, $v_x _{\text{left hand } 4V} = (4) \frac{1}{3+1+10/7} = 0.7368 \text{ V}$</p> <p>With the other voltage source short-circuited and the current source open-circuited, we have $(3+1) \parallel 5 = 2.222 \Omega$</p> <p>$v_{3\Omega} = 4 \frac{2.222}{2.222+2} = 2.105 \text{ V}$. Then, $v_x _{\text{right hand } 4V} = -2.105 \frac{1}{4} = -0.5263 \text{ V}$</p> <p>Finally, with both voltage sources short-circuited, we find that</p> <p>$v_x _{2A} = (1) \left[2 \frac{3}{3+1+10/7} \right] = 1.105 \text{ V}$</p> <p>Adding these three terms together $v_x = 1.316 \text{ V}$</p>	CO2	
	 <p>We define nodal voltage v_1 at the top left node, and nodal voltage v_2 at the top right node. The bottom node is our reference node. By nodal analysis,</p> $-0.02v_1 = \frac{v_1}{10 \times 10^3} + \frac{v_2}{20 \times 10^3} \quad [1]$ $\text{and } v_2 - v_1 = 1 \quad [2]$ <p>Solving,</p> $v_1 = -2.481 \text{ mV} = v_{oc} = V_{TH}$ $R_{TH} = v_{test}/1 = 49.63 \Omega$	CO2	Analysis
	OR		
	<p>State and prove maximum power transfer theorem for network with reactive components.</p> <p>Statement - 1M</p> <p>Proof- 3M</p>	CO2	Knowledge
	 <p>Solution-</p> $-4 + 2 \times 10^3 \left(-\frac{v_x}{4000} \right) + 3 \times 10^3 (0) + v_x = 0$ $v_x = 8 \text{ V} = V_{th}$	CO2	Analysis

	Determination of Isc ----- 2M $R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{8}{0.8 \times 10^{-3}} = 10 \text{ k}\Omega$ I_N=I_{sc} =0.8 mA R_{TH}=10K ohm		
Q3	Attempt any ONE [4M]		
	Compare Series resonance with Anti resonance on the basis of their parameters (at least 4 points) — 4 M OR	CO3	Comprehension
	Far=7.11 KHz -----1.5M Zar=400Kohm-----1.5M Iar=V/Zar= 25micro A-----1M	CO3	Knowledge

===== *