

Total No. of Questions – [03]

Total No. of Printed Pages: 01

G.R. No.

Page code
V239-141(T₁)-IT
V239-121(T₁)-comp

OCTOBER 2019/ INSEM (T1)

S. Y. B.TECH. (COMPUTER ENGINEERING/INFORMATION TECHNOLOGY)
(SEMESTER – III)

COURSE NAME: ANALOG AND DIGITAL ELECTRONICS

COURSE CODE: CSUA21181/ITUA21181

(PATTERN 2018)

Time: [1 Hour]

[Max. Marks: 20]

Instructions to candidates:

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed.
- 4) Assume suitable data where ever required.

Q 1) Attempt any **one**

- a) Explain 1's complement and 2's complement representation with suitable example. [8]
Simplify the Boolean algebraic Expression for designing digital circuits using K-Map:
 $f(A,B,C,D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$
- b) Define standard SOP and POS forms. Simplify the Boolean algebraic expression [8]
for designing digital circuits using Quine-McCluskey Method:
 $f(A,B,C,D) = \sum m(0, 1, 2, 3, 5, 7, 8, 10, 12, 13, 15)$

Q 2) Attempt any **one**

- a) Design 4-bit Binary to Gray code converter using K-Map and draw logic [8]
circuit diagram.
- b) Draw and explain 4-bit BCD adder using binary adder IC 7483. Also explain [8]
three cases of BCD addition using one example each.

Q 3) Attempt any **one**.

- a) Draw the block diagram, truth table and excitation table of JK-Flip Flop. [4]
- b) Convert an S-R Flip-Flop to a J-K Flip-Flop [4]