

Total No. of Printed Pages: 4

G.R. No.	
----------	--

PAPER CODE	VIII-203A
------------	-----------

F.Y. B. TECH. (SEMESTER - I)

COURSE CODE: ET10203A

(PATTERN 2020)


[Max. Marks: 60]

(*) Instructions to candidates:

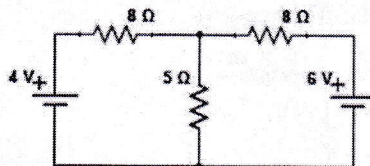- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data where ever required

Solve the following

- i)** For a given network as shown below, considering $5\ \Omega$ as a load resistance, the value of R_{eq} using Thevenin's theorem is [2]



- a) $2\ \Omega$
c) $1.5\ \Omega$
- b) $4.5\ \Omega$
d) $4\ \Omega$

- ii) If two resistances R_1 and R_2 are connected in parallel across a voltage source V_T and total current of circuit is I_T , then current I_2 in resistance R_2 using current division rule is given by following formula [2]

- a) $I_2 = V_T \times [R_2 / (R_1 + R_2)]$ b) $I_2 = I_T \times [R_2 / (R_1 + R_2)]$
c) $I_2 = I_T \times [R_1 / (R_1 + R_2)]$ d) $I_2 = V_T \times [R_1 / (R_1 + R_2)]$

- iii) The load current I_L in a load resistance R_L using Norton's theorem is given by following formula [2]

- a) $I_L = V_N \times R_N / (R_N + R_L)$ b) $I_L = V_N / (R_N + R_L)$
c) $I_L = I_N \times R_N / (R_N + R_L)$ d) $I_L = I_N \times R_L / (R_N + R_L)$

- iv)** In regard to Kirchhoff's Voltage Law (KVL) and concept of loop and circuit, following statement is true: [2]

- a) A loop may contain different circuits and KVL can be applied only to a loop
- b) A circuit may contain different loops and KVL can be applied

only to a circuit

c) A circuit may contain different loops and KVL can be applied only to a loop

d) A loop may contain different circuits and KVL can be applied only to a circuit

v) If Thevenin resistance R_{eq} is 1Ω and Thevenin voltage V_{Th} is 24 V then load current I_L flowing through load resistance R_L of 5Ω is [2]


a) 2 A

b) 6 A

c) 1 A

d) 4 A

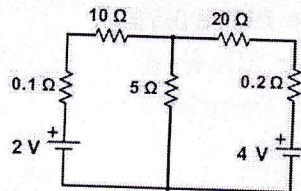vi) For given electric circuit below, consider 5Ω as load resistance. Applying Norton's Theorem to given electric circuit, Norton's Current i.e., Norton's short circuit current (I_N or ISC) and Norton's equivalent resistance R_N are respectively [2]




a) 0.396 A , 4.233Ω

b) 0.396 A , 6.733Ω

c) 0.126 A , 8.788Ω

d) 0.246 A , 8.788Ω

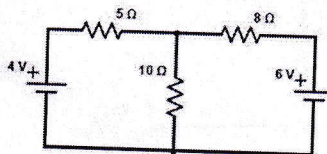vii) For given electric circuit below, current flowing through resistance of 5Ω using Kirchhoff's laws is [2]




a) 0.0706 A

b) 0.0231 A

c) 0.0511 A

d) 0.0921 A

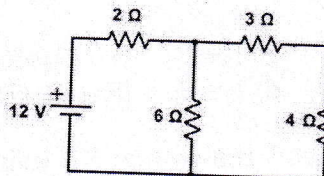viii) For the given circuit below, current flowing through resistance of 4Ω using Superposition theorem is [2]



a) 2 A

b) 2.25 A

c) 1 A

d) Superposition theorem not applicable to this circuit

ix) If $R = 10 \Omega$ and $X_L = 25 \Omega$ then the impedance in rectangular form can be expressed as [2]

a) $(10 - j25) \Omega$

b) $(10 + j25) \Omega$

c) $(10 - j5) \Omega$

d) $(10 + j15) \Omega$

connected to 500 V, calculate (i) maximum value of flux density in the core with 50 Hz supply (ii) voltage induced in the secondary winding and (iii) secondary full load current.

c) A single phase 100 kVA, 1000 V/250 V, 50 Hz transformer has an iron loss of 1 kW. The copper loss when primary carries current of 50 A is 500 W. Determine: - i) area of cross section of the limb if the flux density in the core is 0.9 Tesla and 1000 turns on primary side ii) primary and secondary side full load current iii) the efficiency at full load and 0.8 power factor lagging. [5]

d) A transformer is rated at 90 KVA, at full load its copper losses are 1100W and its iron losses are 950 W. Calculate: [5]
i. Efficiency at full load, unity power factor
ii. Efficiency at 60% of full load, 0.8 power factor

Q.3

Solve any three out of four

a) An electric pump lifts 64m^3 of water per hour to a height of 20 m. If its overall efficiency is 80 %, find the input power of motor. If the pump is used for 2 hours a day, find the daily cost of energy at the rate of Rs. 3/- per unit. [5]

b) A 1500V dc locomotive draws a load of 1200-tonne of mass at 40 km per hour. The tractive resistance of the load is 50 N/tonne and system efficiency is 80 %, calculate the current drawn by the locomotive when the train travels along a level track. [5]

c) In a residential flat, following is the usage of various electrical appliances during a day. [5]

i. 4 fluorescent tubes each of 20 W for 5 hours

ii. 1.5 kW electric geyser for 1 hour

iii. 5 ceiling fans each of 53 W for 6 hours

iv. 800 W electric iron for 45 minutes

v. Other miscellaneous load of 600 W for 3 hours

Estimate the monthly electricity bill for this residential flat for a month of 28 days at the rate of Rs. 3/- per unit.

d) A delta- connected load draws a line current of 15 amperes at a lagging power factor of 0.85 from a 400 V, 50 Hz, 3-phase supply. Find the resistance and inductance of each phase. [5]