

Total No. of Printed Pages: 03

G.R. No.	
----------	--

PAPER CODE	U111-203B
------------	-----------

(PATTERN 2020)

Time: [2Hr]

[Max. Marks: 60]

(*) Instructions to candidates:

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data where ever required

Q.1

- Solve the following
- i) If the a.c. input to a half-wave rectifier is an r.m.s value of $400/\sqrt{2}$ volts, then diode PIV rating is----- [2]
 - a) $400/\sqrt{2}$ V
 - b) 400 V
 - c) $400\sqrt{2}$ V
 - d) 200 V
- ii) Two LED's are connected in series along with limiting resistance. It is supplied with 10 V DC supply and drop across each LED is 2V, the value of limiting resistance for 20 mA current is----- [2]
 - a) 200 Ω
 - b) 250 Ω
 - c) 300 Ω
 - d) 400 Ω
- iii) The internal quantum efficiency of LEDs decreasing _____ with _____ temperature. [2]
 - a) Exponentially, decreasing
 - b) Exponentially, increasing
 - c) Linearly, increasing
 - d) Linearly, decreasing
- iv) For single phase supply frequency of 50 Hz, ripple frequency in full wave rectifier is ---- [2]
 - a) 25 Hz
 - b) 50 Hz
 - c) 100 Hz
 - d) 200 Hz
- v) Each diode in a center-tapped full-wave rectifier is _____ -biased and conducts for _____ of the input cycle. [2]
 - a) forward, 90 degrees
 - b) forward, 180 degrees
 - c) reverse, 90 degrees
 - d) reverse, 360 degrees

- vi) What is the average value of half wave rectifier, for the $V_p(\text{out}) = 50\text{V}$ [2]
 a) 21.2 V b) 15 V
 c) 15.9 V d) 19.9 V
- vii) In Center tapped FWR, if the peak value of secondary voltage is 25 V then the peak value of the output voltage is ____ [2]
 a) 24.3 V b) 11.8 V
 c) 25.7 V d) 12.5 V
- viii) The current flowing through the Photo diode without illumination of light in reverse bias mode is called as ----- [2]
 a) reverse current b) dark current
 c) forward current d) pinch off current
- ix) Determine value of collector current I_C , for $\beta = 150$ and base current $I_B = 430\ \mu\text{A}$. [2]
 a) 100 mA b) 46.8 mA
 c) 64.5 mA d) 80.3 mA
- x) For voltage divider biasing circuit, if $R_1 = 18\ \text{K}\Omega$, $R_2 = 4.7\ \text{K}\Omega$, $V_{CC} = 10\text{V}$. What is the value of V_B (voltage at Base terminal)? [2]
 a) 2.07 V b) 3.23 V
 c) 10 V d) 5.1 V
- xi) In Common Emitter amplifier, if base current is 10 mA and beta is 100. What is the value of collector current? [2]
 a) 1 mA b) 1000 micro A
 c) 1 A d) 10 nano A
- xii) In voltage divider biasing circuit using BJT, if $V_E = 2.42\text{ V}$ and $R_E = 240\Omega$. What is the value of emitter current I_E ? [2]
 a) 10 mA b) 25 mA
 c) 20 mA d) 100 mA
- xiii) What is the total phase shift requirement, around the feedback loop, for a phase-shift oscillator? [2]
 a) 90° b) 180°
 c) 270° d) 360°
- xiv) The biasing circuit has a stability factor of 24. If due to temperature change, I_{CBO} changes by $3\ \mu\text{A}$, then I_C will change by [2]
 a) $8\ \mu\text{A}$ b) $7.2\ \mu\text{A}$
 c) $0.72\ \mu\text{A}$ d) $72\ \mu\text{A}$
- xv) In transistor amplifier circuit, V_{CC} applied as 12 V. For maximum amplification of input signal at its output, what will be the value of V_{CE} required? [2]
 a) 12 V b) 0.7 V
 c) 6 V d) 1.2 V

Q2

Solve any three out of four


- a) Sketch the internal construction of an n-channel Enhancement type MOSFET and explain the pinch off process? [5]

- b) List the MOSFET amplifier configurations, and state two applications for each configuration. [5]
- c) Calculate V_{GS} and V_{DS} for the MOSFET with voltage divider bias circuit, given parameters are $R_1 = 150 \text{ K}\Omega$, $R_2 = 20 \text{ K}\Omega$, $R_D = 200 \Omega$, $V_{DD} = 24 \text{ V}$. Assume this particular MOSFET has minimum values of $I_{D(on)} = 200 \text{ mA}$ at $V_{GS} = 4 \text{ V}$ and $V_{GS(th)} = 2 \text{ V}$. [5]
- d) Sketch the internal structure for TRIAC and draw its complete characteristics. [5]

Q.3

Solve any three out of four

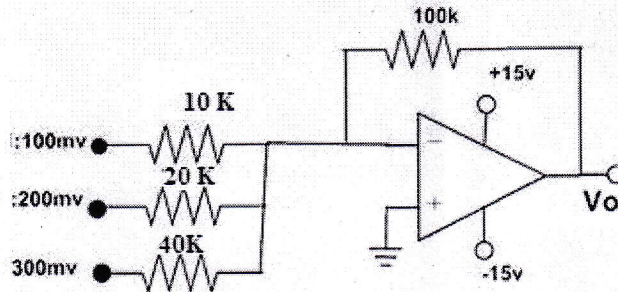- a) Write a short note on CMRR and Slew rate of an op-amp. [5]
- b) Compare between Inverting and noninverting amplifier configurations of an op-amp [5]
- c) Draw the diagram of non-inverting amplifier configuration using an op-amp and derive the expression of its gain. [5]
- d) For the given circuit diagram, if 3 input voltages 100mv; 200mv and 300mv are applied at inverting terminal. Find the output voltage V_o . [5]



-----END-----