

G.R. No.	
----------	--

**DECEMBER 2021 - ENDSEM EXAM**  
**S. Y. B. TECH. (INFORMATION TECHNOLOGY) (SEMESTER - I)**  
**COURSE NAME: DIGITAL ELECTRONICS AND MICROPROCESSOR**  
**COURSE CODE: ITUA21202**  
**(PATTERN 2020)**

Time: [1 Hour]

[Max. Marks: 30]

**Instructions to candidates:**

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4, Q.5 OR Q.6.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

- Q.1) a) Design Mod 75 counter using IC 7490 [4]  
b) Design 3-bit Synchronous Down Counter using JK-Flip Flop [6]  
OR
- Q.2) a) Compare Moore and Mealy machines [4]  
b) Design 4-bit Ring and Johnson counter [6]
- Q.3) a) List characteristics of digital IC's and explain Voltage parameters [4]  
b) Design and implement BCD to excess-3 code converter using PAL [6]  
OR
- Q.4) a) Draw and Elaborate diagram of TTL to CMOS interfacing [4]  
b) Draw and Discuss working of 2 input CMOS NAND gate [6]
- Q.5) a) List the uses of Program counter and Stack pointer in 8085 Microprocessor [4]  
b) Conclude the Modelling Styles used for VHDL language with example [6]  
OR
- Q.6) a) Determine the status of flag register after addition of 07H and CFH [4]  
b) Conclude Data transfer instructions with examples [6]