

Total No. of Questions – [3]

Total No. of Printed Pages: 04

G.R./PRN No.	
-----------------	--

PAPER CODE	U112-203B (Reg)
---------------	-----------------

**DECEMBER 2022 (INSEM+ ENDSEM) EXAM**

**F.Y. B. TECH. (SEMESTER - I)**

**COURSE NAME: BASIC ELECTRONICS ENGINEERING**

**COURSE CODE: ET10203B**

**(PATTERN 2020)**

Time: [2Hr]

[Max. Marks: 60]


**(\*) Instructions to candidates:**

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data where ever required

Question No.	Question Description	Marks	CO mapped	Blooms Taxonomy Level
Q.1	i) Determine the peak output voltage for the full wave bridge rectifier. Assume silicon diode. The transformer is specified to have a 10 V rms secondary voltage and 120 V across the primary winding. a) 8.6 V b) 12.74 V c) 14.14 V d) 13.44 V	[2]	CO1	Apply
	ii) The potential drop in full wave bridge rectifier is _____ a) 1.1V b) 1.2V c) 1.3V d) 1.4V	[2]	CO1	Apply
	iii) What happens to the diode when the positive voltages are applied at anode? a) Diode gets forward biased b) Diode begin to conduct c) Depletion region becomes smaller d) All of the above	[2]	CO1	Understand
	iv) A forward potential of 10V is applied to a Si diode. A resistance of 10 K $\Omega$ is also in series with the diode (Assume practical diode	[2]	CO1	Apply

model). The current is----- a) 0.93 mA b) 10 mA c) 1 mA d) 0.7 mA			
v) Semiconductor undergoing the process of doping are classified as a) intrinsic semiconductor b) extrinsic semiconductor c) both a and b d) none of the above	[2]	CO1	Understand
vi) Unidirectional current of diode is termed as _____ a) Amplification b) modulation c) rectification d) none of the above	[2]	CO1	Understand
vii) The cut in or the Knee voltage of the silicon diode is _____ a) 1V b) 0.5V c) 0.7V d) 0.8V	[2]	CO1	Understand
viii) _____ is the maximum reverse potential that a diode can withstand a) Maximum power dissipation b) Forward voltage drop c) Peak inverse voltage d) Average forward current	[2]	CO1	Understand
ix) The current gain ( $\beta$ ) of a transistor in common emitter configuration is 40. If the collector current changes by 160 mA, then required change in the base current is .....for constant $V_{CE}$ a) 4 mA b) 0.4 mA c) 40 mA d) 4 A	[2]	CO2	Apply
x) In a fixed bias circuit silicon NPN transistor (CE) with $\beta = 90$ is used. If $V_{cc} = 15\text{ V}$ , $R_c = 3\text{ K}\Omega$ and $R_b = 1\text{ M}\Omega$ , the $V_{CE}$ at Q-point is given as: a) 12.41 V b) 7.5 V c) 10 V d) 11.6 V	[2]	CO2	Apply

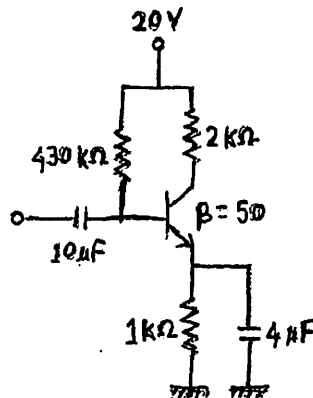xi) Determine saturation current for the following circuit:  
 $(V_{CE(sat)} = 0.2 \text{ V}, V_{BE} = 0.7 \text{ V})$



- a) 10 mA
- b) 6.67 mA
- c) 20 mA
- d) 0 mA

xii) Which of the following method of biasing provides the best operating point stability?

- a) Two battery bias
- b) Base bias
- c) Collector feedback bias
- d) Voltage divider bias

xiii) In NPN transistor, operating in saturated mode, the value of output voltage  $V_{CE}$  is \_\_\_\_\_

- a) Less than  $V_{BE}$
- b) Greater than  $V_{BE}$
- c) Less than  $2V_{BE}$  and greater than  $V_{BE}$
- d) Equal to  $V_{BE}$

xiv) In how many regions can the biased transistor work

- a) Four
- b) Two
- c) Three
- d) Five

xv) Calculate the value of emitter current for a transistor with  $\alpha_{dc} = 0.98$ ,  $I_{CBO} = 5 \mu\text{A}$  and  $I_B = 95 \mu\text{A}$ .

- a) 4.5 mA
- b) 4 mA
- c) 3.5 mA
- d) 5 mA

[2]

CO2

Apply

[2]

CO2

Understand

[2]

CO2

Understand

[2]

CO2

Understand

[2]

CO2

Apply

Q2	<p><b>Solve any three out of four</b></p> <p>a) Calculate <math>V_{GS}</math> and <math>V_{DS}</math> for the circuit, with <math>R_1=100\text{ K}\Omega</math>, <math>R_2=20\text{ K}\Omega</math>, <math>R_D=100\text{ }\Omega</math>, <math>R_S=0\text{ }\Omega</math>, <math>V_{DD}=25\text{ V}</math>. Assume this particular MOSFET has minimum values of <math>I_{D(on)}=300\text{ mA}</math> at <math>V_{GS}=4\text{ V}</math> and <math>V_{GS(th)}=1.5\text{ V}</math>.</p> <p>b) Sketch internal structure and V-I characteristics of TRIAC and explain its working?</p> <p>c) Sketch n-channel MOSFET constructional diagram and explain the pinch-off process?</p> <p>d) With the help of V-I characteristics of SCR, explain the turn-on process for SCR?</p>	[5]	CO3	Apply
		[5]	CO3	Understand
		[5]	CO3	Understand
		[5]	CO3	Understand
Q.3	<p><b>Solve any three out of four</b></p> <p>a) Calculate closed loop gain of the circuit shown below and find out its output voltage if <math>2.5\text{ Vdc}</math> input is applied to the circuit</p> <div data-bbox="501 868 893 1123" data-label="Diagram"> </div> <p>b) With the help of diagram explain the working of OPAMP as non-inverting comparator?</p> <p>c) Calculate the output voltage for the circuit shown in the figure</p> <div data-bbox="396 1319 984 1613" data-label="Diagram"> </div> <p>d) With the help of suitable diagram explain the following</p> <ol style="list-style-type: none"> <li>Slew rate</li> <li>Virtual ground</li> </ol>	[5]	CO4	Analyze
		[5]	CO4	Understand
		[5]	CO4	Analyze
		[5]	CO4	Understand