

G.R. No.

PAPER CODE

0111-203A(REF)

MAY 2022 (INSEM+ ENDSEM) EXAM
F.Y. B. TECH. (SEMESTER - II)
COURSE NAME: BASIC ELECTRICAL ENGINEERING
COURSE CODE: ET10203A
(PATTERN 2020)

Time: [2Hr]

[Max. Marks: 60]

(*) Instructions to candidates:

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed.
- 3) Use suitable data wherever required.

Q.1

Solve the following

i) For a given network as shown in Fig.1, considering 4Ω as a load resistance, the value of R_{eq} using Thevenin's theorem is

- | | |
|---------------|---------------|
| a) 14Ω | b) 15Ω |
| c) 16Ω | d) 17Ω |

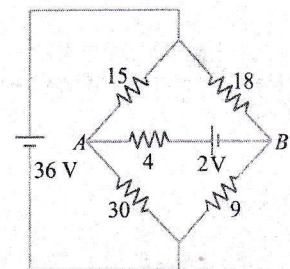


Fig.1

ii) A battery of 24V is applied across terminals AB of the circuit shown in Fig. 2. The current in 2Ω resistor will be

- | | |
|----------|----------|
| a) 3 A | b) 6 A |
| c) 2.5 A | d) 1.5 A |

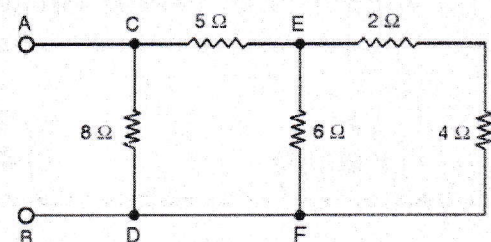


Fig.2

iii) For a given network as shown in Fig.3, considering 1Ω as a load resistance, the value of I_N using Norton's theorem is

- | | |
|----------|----------|
| a) 1.5 A | b) 2.5 A |
| c) 3.5 A | d) 4.5 A |

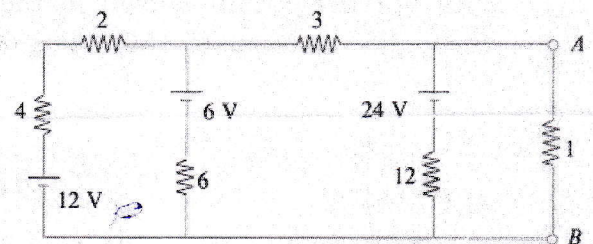


Fig.3

iv) Referring to Fig.4, the total circuit resistance will be

- a) 1000 Ω b) 400 Ω
c) 1400 Ω d) 135 Ω

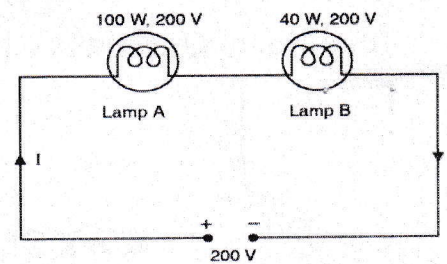


Fig.4

v) Three equal resistors are connected as shown in the Fig.5. Find the equivalent resistance between points A and B.

- a) 3R b) R/3
c) 3R/2 d) 2R/3

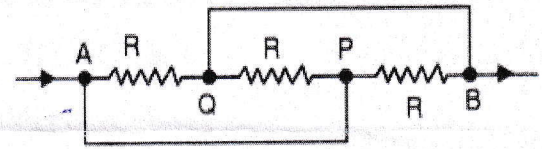


Fig.5

vi) Applying Norton's Theorem to the circuit shown in Fig.6, the short circuit current (I_N or I_{SC}) and Norton's equivalent resistance R_N are respectively

- a) 11.11 A, 9 Ω b) 13.33 A, 9 Ω
c) 11.11 A, 6 Ω d) 13.33 A, 6 Ω

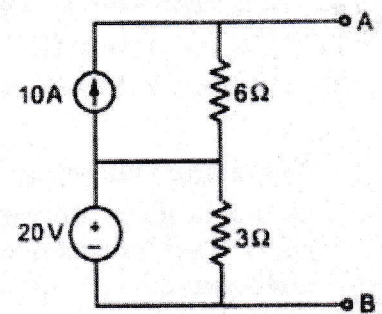


Fig.6

vii) For given electric circuit in Fig. 7, current flowing through resistance of 20 Ω using Kirchhoff's laws is

- a) 1.11 A b) 2.22 A
c) 3.33 A d) 4.44 A

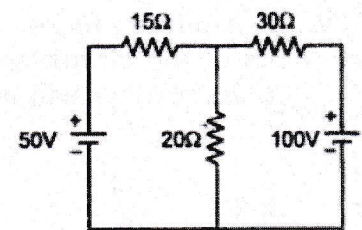


Fig.7

viii) For the circuit shown in the Fig. 8, current flowing through resistance of 15 Ω using Superposition theorem is due to source S1 only will be

- a) 1.7142 A b) 2.2587 A
c) 3.4562 A d) none of the above

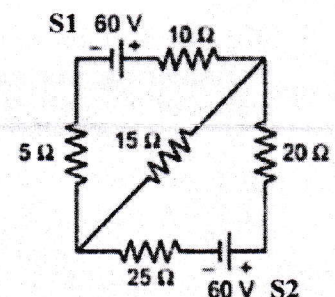


Fig.8

ix) If $R=15 \Omega$ and $X_L=55 \Omega$, then the impedance in rectangular form can be expressed as

- a) $(15 - j55) \Omega$ b) $(15 + j55) \Omega$

- x)** An alternating current, $i=414\sin(100\pi t)$ A is passed through a series circuit consist of $R=100\ \Omega$ & inductance of 0.31831 What will be expression for the instantaneous value of the voltage across i) inductance and ii) combination [2]
- a) $V_L=141.4 \sin(100\pi t + 90^\circ)$, $V=200 \sin(100\pi t + 45^\circ)$
 b) $V_L=141.4 \sin(100\pi t + 45^\circ)$, $V=200 \sin(100\pi t + 90^\circ)$
 c) $V_L=200 \sin(100\pi t + 90^\circ)$, $V=141.4 \sin(100\pi t + 45^\circ)$
 d) $V_L=200 \sin(100\pi t + 90^\circ)$, $V=141.4 \sin(100\pi t + 45^\circ)$

- xi)** The voltage and current of the circuit is given by; [2]

$$e = 120 \sin(314t), i = 10 \sin(314t + \pi/6)$$

 Calculate values of R and C which are connected in series to form circuit.
 a) $10.393\ \Omega$, $276.77\ \mu\text{F}$ b) $16.873\ \Omega$, $644.76\ \mu\text{F}$
 c) $20.393\ \Omega$, $740.50\ \mu\text{F}$ d) $10.393\ \Omega$, $530.45\ \mu\text{F}$

- xii)** A series circuit having pure resistance of $40\ \Omega$, pure inductance of $50.07\ \text{mH}$, and capacitor is connected across a $400\ \text{V}$, $50\ \text{Hz}$, AC supply. This combination draws a current of $10\ \text{A}$. The power factor of circuit and capacitor value is respectively [2]
 a) $0.92\ \text{lag}$, $20.10 \times 10^{-3}\ \text{F}$ b) $0.92\ \text{lead}$, $20.10 \times 10^{-3}\ \text{F}$
 c) 1 , $2.023 \times 10^{-4}\ \text{F}$ d) 1 , $2.023 \times 10^{-6}\ \text{F}$

- xiii)** A series RLC circuit is connected to $230\ \text{V}$ ac supply. The current drawn by circuit at resonance is $25\ \text{A}$ and voltage drop across capacitor is $4000\ \text{V}$. Calculate resonant frequency and inductance value if capacitance is $5\ \mu\text{F}$. [2]
 a) $180.567\ \text{Hz}$, $0.111\ \text{H}$ b) $198.943\ \text{Hz}$, $0.128\ \text{H}$
 c) $200.954\ \text{Hz}$, $0.168\ \text{H}$ d) $150.563\ \text{Hz}$, $0.156\ \text{H}$

- xiv)** If $V_1 = 4+j3$ volts and $V_2 = 5+j6$ volts, the product $V_1 \times V_2$ in volts as expressed in polar form will be [2]
 a) $0.64 \angle -13.32$ b) $39.05 \angle 87.06$
 c) $7.81 \angle 50.19$ d) $7.81 \angle -50.19$

- xv)** In a series RLC circuit at resonance, the magnitude of the voltage developed across the capacitor [2]
 (a) is always zero.
 (b) can never be greater than the input voltage.
 (c) can be greater than input voltage and it is 90° out of phase with the input voltage.
 (d) is in phase with the input voltage.

Q2

Solve any three out of four

- a)** For a single phase transformer having primary and secondary turns of 440 and 880 respectively, determine the transformer kVA rating if half load secondary current is $7.5\ \text{A}$ and maximum value of core flux is $2.25\ \text{mWb}$. [5]
- b)** The iron loss of $100\ \text{kVA}$, $1000/250\ \text{V}$, single phase $50\ \text{Hz}$, transformer is $1000\ \text{W}$. The copper loss when primary carries current of $50\ \text{A}$ is $500\ \text{W}$. Find i) Area of cross-section of limb if working flux density is $0.9\ \text{T}$ and primary has 1000 turns ii) Primary and secondary currents iii) Efficiency at full-load and 0.3 power factor. [5]

c) A single phase 100 kVA, 3.3 kV/230 V, 50 Hz transformer has 89.5% efficiency at 0.85 lag pf. both at full load and also at half load. Determine the efficiency of the transformer at 75% load and 0.9 lead pf.

[5]

d) The no load and full load unity power factor readings of direct loading test on single phase transformer are as given below. Find its % efficiency and % voltage regulation at full load and unity pf.

[5]

	Primary Side			Secondary Side	
	V ₁	I ₁	W ₁	V ₂	I ₂
No load Test	220V	1.65A	75W	110V	0A
Full load unity p.f	220V	18A	3700W	102.5A	35A

Q.3

Solve any three out of four

a) A pump driven by an electric motor lifts 1.5 m³ of water per minute to a height of 40 m. The pump has an efficiency of 90% and motor has an efficiency of 85%. Determine: (a) the power input to the motor. (b) The current taken from 480 V supply. (c) The electric energy consumed when motor runs at this load for 4 hours. Assume mass of 1 m³ of water to be 1000 kg.

[5]

b) A 3 tonne electric motor operated vehicle is being driven at a speed of 24 km/hr upon an incline of 1 in 20. The tractive resistance may be taken as 20 kg per ton. Assuming a motor efficiency of 85% and the mechanical efficiency between the motor and road wheels of 80%, calculate (a) the output of the motor (b) the current taken by motor if it gets power from a 220 V source. (c) the cost of energy for a run of 48 km, taking energy charge as 40 paise/kWh.

[5]

c) A factory has a 240V supply from which the following loads as (a) Lighting: 300 lamps of 150W, 400 lamps of 100W, 500 lamps of 60W lamps, lighting load is for 4 hours/day, (b) Heating: 100kW for 10 hours/day, (c) Motors: 44.76kW with efficiency of 75% for 2 hours/day, (d) Miscellaneous: Various load taking a current of 40 A for 2 hours/day. Calculate the weekly consumption of the factory in kWh when working on a 5 days week. What current is taken when the lighting load only is switched on?

[5]

d) Three inductive coils each having resistance of 16 Ω and reactance of 12 Ω are connected in star across a 400 V, three-phase, 50 Hz supply. Calculate : i) Phase voltage ii) Line current iii) Phase current iv) Power factor v) Total Power consumed

[5]