

Total No. of Questions – [3]

Total No. of Printed Pages: 02

G.R. No.

PAPER CODE **U222-243(ESE)**

**May 2022 (ENDSEM) EXAM**  
**S.Y. B. TECH. (SEMESTER - II) E&TC**  
**COURSE NAME: ANALOG CIRCUITS**  
**COURSE CODE: ETUA22203**

**(PATTERN 2020)**

Time: [1Hr]

[Max. Marks: 30]

**(\*) Instructions to candidates:**

- 1) **Figures to the right indicate full marks.**
- 2) **'a' part of every question is compulsory**
- 3) **Use of scientific calculator is allowed**
- 4) **Use suitable data where ever required**

Q.1 a) Discriminate between active and passive filters with the help of various electronics parameters [4]

b) Sketch the circuit diagram of second order Butterworth Low Pass Filter. Also draw the frequency response graph of it and write the formula to calculate its cut off frequency. [6]

**OR**

b) Calculate the gain of first order LPF and second order LPF at frequencies 100 Hz and 2KHz. Cut off frequency  $f_H = 1$  KHz and maximum gain of the filter is 10. [6]

Q2 a) A 5 bit R-2R ladder network with reference voltage of 10 V is given. Calculate: 1) Full scale output voltage for digital input 11111 2) Output voltage for digital input 11001. [4]

b) Sketch the neat circuit diagram for Voltage To Current Converter with Grounded Load and derive the complete expression for the load current ( $I_L$ ). [6]

**OR**

b) Sketch the neat circuit diagram of 2 bit Flash ADC and explain its working along with advantages and disadvantages. [6]

Q.3

a) For a PLL 565, the free running frequency is 2.5 KHz,  $+V_{CC} = +10V$ ,  $-V_{EE} = -10V$ . If demodulation capacitor  $C_2 = 10\mu F$ . Calculate Lock range and Capture range. [4]

b) Sketch the block diagram of basic Phase Lock Loop (PLL) and give the significance of each block. [6]

OR

b) Justify with block diagram that how PLL is used as FM demodulator. [6]