

Total No. of Questions – [4]

Total No. of Printed Pages: 4

G.R./PRNNo.

PAPER  
CODE

U123-203A (REG)

**MAY 2023 (INSEM+ ENDSEM) EXAM****F.Y. B. TECH. (SEMESTER - II)****COURSE NAME: BASIC ELECTRICAL ENGINEERING****COURSE CODE: ET10203A****(PATTERN 2020)**


Time: [2Hr]

[Max. Marks:

60]

**(\*) Instructions to candidates:**

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data where ever required

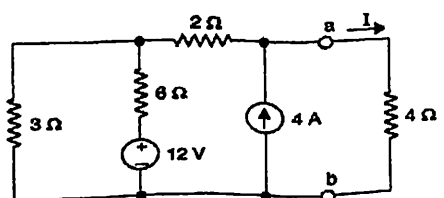Question No.	Question Description	Marks	CO mapped	Blooms Taxonomy Level
Q.1	<p>i) For the circuit shown in Fig.1, the open circuit voltage across the terminals a and b after removing <math>4\ \Omega</math> resistance from the circuit is</p>  <p style="text-align: center;">Fig.1</p> <p>a) 16 V      b) 4 V      c) 12 V      d) 20 V</p> <p>ii) For the circuit shown in Fig.1, the equivalent resistance seen by the open terminals a and b after removing <math>4\ \Omega</math> resistance and disabling all the sources in the network is</p> <p>a) 1.636 <math>\Omega</math>      b) 1 <math>\Omega</math>      c) 4 <math>\Omega</math>      d) 11 <math>\Omega</math></p> <p>iii) For the circuit shown in Fig.1, the voltage drop across <math>4\ \Omega</math> resistance will be</p> <p>a) 10 V      b) 20 V      c) 30 V      d) 15 V</p> <p>iv) For the circuit shown in Fig.1, the short circuit current flowing through the terminals a and b after removing <math>4\ \Omega</math> resistance from the circuit is</p> <p>a) 4 A      b) 5 A      c) 10 A      d) 0 A</p>	[2]	1	Apply
		[2]	1	Apply
		[2]	1	Apply
		[2]	1	Apply

<p>v) For a circuit shown in Fig. 1, the current in flowing through <math>4\ \Omega</math> resistance is</p> <p>a) 5 A      b) 10 A      c) 2.5 A      d) 0 A</p>	[2]	1	Apply
<p>vi) For a circuit shown in Fig.1, the current flowing through <math>4\ \Omega</math> resistance due to 12 V voltage source acting alone will be</p> <p>a) 5 A      b) 0 A      c) 0.5 A      d) 2.5 A</p>	[2]	1	Apply
<p>vii) For a circuit shown in Fig.1, the current flowing through <math>4\ \Omega</math> resistance due to 4 A current source acting alone will be</p> <p>a) 2 A      b) 2.5 A      c) 0.5 A      d) 0 A</p>	[2]	1	Apply
<p>viii) The current shown by ammeter for a circuit shown in Fig.2 in the branch containing <math>3\ \Omega</math> resistance in series with 2 V voltage source is</p> <div data-bbox="608 578 972 764" data-label="Diagram"> </div> <p>Fig. 2</p> <p>a) 0 A      b) 1 A      c) 1.5 A      d) 2.5 A</p>	[2]	1	Apply
<p>ix) A sinusoidal voltage is given by the expression <math>v = 100 \sin(\omega t + \theta)</math> Volts. At <math>t = 0</math>, the instantaneous value of voltage is found to be 50 Volts. The time at which the voltage will reach its positive maximum will be _____ ms if the frequency of the supply is 50 Hz.</p> <p>a) 5      b) 3.33      c) 1.67      d) 6.66</p>	[2]	2	Apply
<p>x) The average value of a current over a half cycle is found to be 10 A. The amplitude and rms value of this current in amperes must be respectively</p> <p>a) 10, 11.1      b) 15.7, 10      c) 15.7, 11.1      d) 11.1, 15.7</p>	[2]	2	Underst and
<p>xi) When a pure capacitance of <math>100\ \mu\text{F}</math> is connected across a single phase, 230 V, 50 Hz, ac supply, the expression for current is</p> <p>a) <math>i = 10.22 \sin(314t + 90^\circ)</math> A      b) <math>i = 7.22 \sin(314t + 90^\circ)</math> A  c) <math>i = 10.22 \sin(314t - 90^\circ)</math> A      d) <math>i = 7.22 \sin(314t - 90^\circ)</math> A</p>	[2]	2	Apply
<p>xii) If an apparent power drawn by a series R-L circuit is 1300 VA while the active power is 1200 W when connected across a single phase, 300 V, 50 Hz ac supply, the inductive reactance connected in the circuit in <math>\Omega</math> will be</p> <p>a) 75      b) 69.23      c) 63.90      d) 26.61</p>	[2]	2	Apply
<p>xiii) A resistance of <math>100\ \Omega</math> and capacitance of <math>50\ \mu\text{F}</math> are connected in series across a 200 V, 50 Hz ac supply. The voltage in Volts across the capacitor will be</p> <p>a) 123.5      b) 168.7      c) 200      d) 107.4</p>	[2]	2	Apply

	<p>xiv) A resistance of <math>20\ \Omega</math> and an inductance of <math>20\ \text{mH}</math> are connected in series across a single phase, <math>200\ \text{V}</math>, <math>50\ \text{Hz}</math> ac supply. The reactive power in VAR will be  a) 571.85      b) 1908.06      c) 1820.35      d) 1143.7</p> <p>xv) A series circuit consisting of a resistance of <math>100\ \Omega</math>, an inductor of inductance <math>0.6\ \text{H}</math> and a variable capacitor connected across a single phase, <math>220\ \text{V}</math>, <math>50\ \text{Hz}</math> ac supply. The value of the capacitance of the capacitor at which the current in the circuit will reach its maximum is  a) <math>16.88\ \text{nF}</math>      b) <math>16.88\ \text{mF}</math>      c) <math>16.88\ \text{F}</math>      d) <math>16.88\ \mu\text{F}</math></p>	[2]	2	Apply
		[2]	2	Apply
Q2	<p><b>Solve any three out of four</b></p> <p>a) A 30 KVA, 2000/200 V, 50 Hz, single phase transformer has a full load copper losses of 787.5 W on high voltage side and 337.5 W on low voltage side. Determine i) the high voltage and low voltage winding resistances ii) the equivalent resistance referred to low voltage side.</p> <p>b) A 200 kVA, 50 Hz, single phase transformer has an efficiency of 95 % on full load at 0.8 power factor and on half load at 0.8 power factor. Determine its percentage efficiency at unity power factor under the loading condition of 75 % of its full load.</p> <p>c) The resistance and leakage reactance of a single phase 10 KVA, 2200/220 V distribution transformer are as given below.  High voltage (HV winding):- <math>r_1 = 4\ \Omega</math>, <math>x_1 = 5\ \Omega</math>  Low voltage (LV winding):- <math>r_2 = 0.04\ \Omega</math>, <math>x_2 = 0.05\ \Omega</math>  The transformer is supplying rated KVA at 0.8 power factor lagging to a load at rated voltage. Determine the % voltage regulation. At what power factor will the % voltage regulation be zero?</p> <p>d) Draw the exact equivalent circuit of a single phase transformer and state various types of losses that occur in case of a single phase transformer.</p>	[5]	3	Apply
		[5]	3	Apply
		[5]	3	Apply
		[5]	3	Underst and
Q.3	<p><b>Solve any three out of four</b></p> <p>a) Three coils each of resistance <math>100\ \Omega</math> and an inductance of <math>0.211\ \text{Henry}</math> are connected in delta across a symmetrical three phase, <math>440\ \text{V}</math>, <math>50\ \text{Hz}</math> ac supply. Calculate i) phase current ii) phase voltage iii) line current iv) active power consumed in kW (upto 3 digits after the decimal point) v) reactive power in kVAR (upto 3 digits after the decimal point)</p> <p>b) Draw a neat phasor diagram for a three phase balanced star connected capacitive type of load in each phase across a symmetrical three phase ac supply and hence derive the relationship between the line voltage and phase voltage.</p>	[5]	4	Apply
		[5]	4	Apply

	<p>c) An electrically driven pump lifts <math>80 \text{ m}^3</math> of water per minute and consumes total electrical energy of <math>16817.4 \text{ kWh}</math> for a month of 30 days when operates for 2 hours per day. The efficiencies of motor and pump are 70 % and 80 % respectively. Calculate the height to which water is raised by the pump. Assume <math>1 \text{ m}^3</math> of water to weigh 1000 kg and take 'g' as <math>9.81 \text{ m/s}^2</math>.</p>	[5]	4	Apply
	<p>d) An electric hoist makes 10 double journeys per hour. In each journey, a load of 6 tonnes is raised to a height of 60 meters in 90 seconds. The hoist cage weights 0.5 tonne when empty while the counter-weight weighs 3 tonnes. The efficiency of the hoist is 80 % and of the driving motor 88 %. Calculate i) electric energy absorbed per double journey ii) hourly energy consumption in kWh iii) cost of electrical energy consumption if the hoist works for 4 hours/day for 30 days. Cost per kWh of electricity is 50 paise. Take 'g' as <math>9.81 \text{ m/s}^2</math>.</p>	[5]	4	Apply