

Total No. of Questions – [3]

Total No. of Printed Pages: 04

G.R. No.	
----------	--

PAPER CODE	U/23-203B(Reg)
------------	----------------

MAY 2023 (INSEM+ ENDSEM) EXAM
F.Y. B. TECH. (SEMESTER - II)
COURSE NAME: BASIC ELECTRONICS ENGINEERING
COURSE CODE: ET10203B

(PATTERN 2020)

Time: [2Hr]

[Max. Marks: 60]



(*) Instructions to candidates:

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data where ever required

Ques tion No.		Question Description	Marks	CO mapp ed	Blooms Taxonomy Level
Q.1	i)	Solve the following If the a.c. input to a half-wave rectifier is an r.m.s value of $200/\sqrt{2}$ volts, then diode PIV rating is----- a) $200/\sqrt{2}$ V b) 400 V c) $200 \sqrt{2}$ V d) 200 V	[2]	CO1	Apply
	ii)	Two LED's are connected in series along with limiting resistance. It is supplied with 10 V DC supply and drop across each LED is 2V, the value of limiting resistance for 10 mA current is----- a) 200Ω b) 250Ω c) 600Ω d) 400Ω	[2]	CO1	Apply
	iii)	In RC phase shift oscillator producing output at $f = 500$ Hz, $R = 7.5$ Kohm then $C =$ ----. a) 0.01 micro F b) 0.017 micro F c) 0.012 nF d) 0.001 micro F	[2]	CO1	Apply

iv)	For single phase supply frequency of 60 Hz, output signal frequency in full wave rectifier is ---- a) 25 Hz b) 50 Hz c) 120 Hz d) 200 Hz	[2]	CO1	Apply
v)	Each diode in a center-tapped full-wave rectifier is _____-biased and conducts for _____ of the input cycle. a) forward, 90 degree b) forward, 180 degree c) reverse, 90 degree d) reverse, 360 degree	[2]	CO1	Apply
vi)	What is the average value of half wave rectifier, for $V_p(\text{out}) = 50\text{V}$ a) 21.2 V b) 15 V c) 15.9 V d) 19.9 V	[2]	CO1	Apply
vii)	In Center tapped FWR, if the peak value of secondary voltage is 25 V then the peak value of the output voltage is ____ a) 24.3 V b) 11.8 V c) 25.7 V d) 12.5 V	[2]	CO1	Apply
viii)	The current flowing through the Photo diode without illumination of light in reverse bias mode is called as ----- a) reverse current b) dark current c) forward current d) pinch off current	[2]	CO1	Understand
ix)	Determine value of collector current I_c , for $\beta = 180$ and base current $I_B = 340 \mu\text{A}$. a) 61.2 mA b) 46.8 mA c) 64.5 mA d) 80.3 mA	[2]	CO2	Apply
x)	For voltage divider biasing circuit, if $R_1 = 18 \text{ K}\Omega$, $R_2 = 4 \text{ K}\Omega$, $V_{CC} = 10\text{V}$. What is the value of V_B (voltage at Base terminal)? a) 2.07 V b) 1.81V c) 10 V d) 5.1 V	[2]	CO2	Apply
xi)	A forward potential of 10V is applied to a Si diode. A resistance of $10 \text{ K}\Omega$ is also in series with the diode. The current is----- (Assume Si diode practical model) a) 0.93 mA b) 10 mA c) 1 mA d) 0.7 mA	[2]	CO2	Apply

	xii)	In voltage divider biasing circuit using BJT, if $V_E=2.42\text{ V}$ and $R_E=240\ \Omega$, What is the value of emitter current I_E ? a) 10 mA b) 25 mA c) 20 mA d) 100 mA	[2]	CO2	Apply
	xiii)	What is the total phase shift requirement for a RC phase-shift oscillator? a) 90° b) 180° c) 270° d) 360°	[2]	CO2	Apply
	xiv)	The biasing circuit has a stability factor of 24. If due to temperature change, I_{CBO} changes by $3\ \mu\text{A}$, then I_C will change by a) $8\ \mu\text{A}$ b) $7.2\ \mu\text{A}$ c) $0.72\ \mu\text{A}$ d) $72\ \mu\text{A}$	[2]	CO2	Apply
	xv)	ix) Determine value of collector current I_C , for $\beta=200$ and base current $I_B=40\ \mu\text{A}$. a) 8 Amp b) 8000 mA c) 8 mA d) $80\ \mu\text{A}$	[2]	CO2	Apply
Q2	a)	Solve any three out of four questions. Sketch the internal construction of an n-channel Enhancement type MOSFET and explain the pinch off process?	[5]	CO3	Understand
	b)	Draw voltage divider biasing CS amplifier circuit using n channel E-MOSFET and Explain the significance of coupling and bypass capacitors connected in the circuit.	[5]	CO3	Understand
	c)	Calculate V_{GS} and V_{DS} for the MOSFET with voltage divider bias circuit, given parameters are $R_1 = 150\text{ K}\Omega$, $R_2 = 20\text{ K}\Omega$, $R_D = 200\ \Omega$, $V_{DD} = 24\text{ V}$. Assume this particular MOSFET has minimum values of $I_{(on)} = 200\text{ mA}$ at $V_{GS} = 4\text{ V}$ and $V_{GS(th)} = 2\text{ V}$.	[5]	CO3	Apply
	d)	Sketch the forward characteristics of SCR for different values of gate current and explain turn on process of it.	[5]	CO3	Understand
Q.3	a)	Solve any three out of four questions. Explain the following terms related to a differential amplifier with necessary diagrams i) Virtual ground ii) Slew Rate	[5]	CO4	Understand

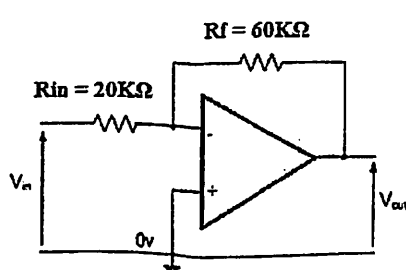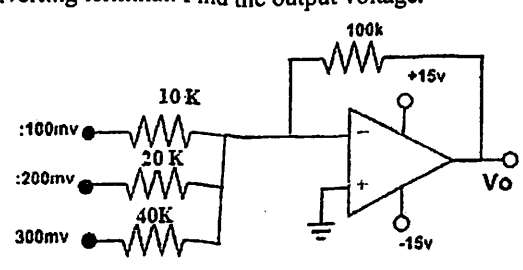	b)	Compare between Inverting and Non-inverting amplifier configurations of an op-amp.	[5]	CO4	Understand
	c)	<p>Calculate closed loop gain of the circuit shown below and find out its output voltage if 3V DC input is applied to the circuit.</p> 	[5]	CO4	Apply
	d)	<p>If 3 input voltages 100mv; 200mv and 300mv are applied at inverting terminal. Find the output voltage.</p> 	[5]	CO4	Apply