

Total No. of Printed Pages: 4

G.R./PRN No.	
-----------------	--

PAPER CODE	0123-203A(RF)
---------------	---------------

**F.Y. B. TECH. (SEMESTER – II)**

**COURSE CODE: ET10203A**

**(PATTERN 2020)**

Time: [2Hr]

[Max. Marks: 60]

**(\*) Instructions to candidates:**

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data wherever required

Question No.	Question Description	Marks	CO mapped	Blooms Taxonomy Level
Q.1	<p><b>Solve the following</b></p> <p>i) The current flowing through the branch ab is _____ when 30 V source acting alone for the circuit shown in Figure 1.</p> <p style="text-align: center;">Figure 1</p> <p>(a) 2 A                      (b) 3 A                      (c) 1 A                      (d) 0</p> <p>ii) The current flowing through the branch ab is _____ when 12 A source acting alone for the circuit shown in Figure 1.</p> <p>(a) 2 A                      (b) 3 A                      (c) 1 A                      (d) 4 A</p> <p>iii) While applying Thevenin's Theorem to a given network, the equivalent resistance is obtained by _____</p> <p>(a) Shorting all voltage sources  (b) Opening all current sources  (c) Shorting all voltage sources and opening all current sources  (d) Opening all voltage sources and shorting all current sources</p> <p>iv) An ideal voltage source is one that _____</p> <p>(a) has high internal resistance  (b) provides constant voltage irrespective of current  (c) supplies constant current  (d) delivers constant power</p>	<p>[2]</p> <p>[2]</p> <p>[2]</p> <p>[2]</p>	<p>CO1</p> <p>CO1</p> <p>CO1</p> <p>CO1</p>	<p>Apply</p> <p>Apply</p> <p>Understand</p> <p>Understand</p>

v) Find the Thevenin's Voltage source value when branch AB acts as the load for the circuit shown in Figure 2. All resistance values are in  $\Omega$ .

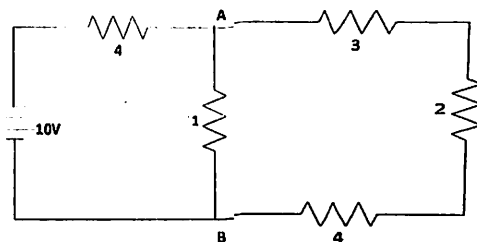


Figure 2

- (a) 6.92 V (b) 3.08 V (c) 10 V (d) 2 V

vi) What is the value of equivalent resistance observed from terminals A and B in case of the circuit shown in Figure 3? All resistance values are in  $\Omega$ .

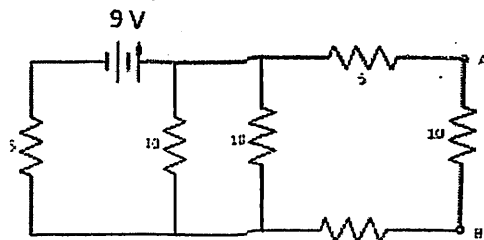


Figure 3

- (a) 10  $\Omega$  (b) 12.5  $\Omega$  (c) 3.75  $\Omega$  (d) 20  $\Omega$

vii) What is the value of Thevenin's Voltage when 10  $\Omega$  is opened as a load resistance in case of the circuit shown in Figure 4? All resistance values are in  $\Omega$ .

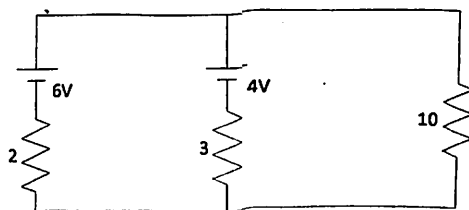


Figure 4

- (a) 10 V (b) 2 V (c) 5.2 V (d) 4.8 V

viii) The current in 10  $\Omega$  resistance for the circuit shown in Figure 4 will be

- (a) 4.33 A (b) 0.52 A (c) 0.557 A (d) 0.464 A

ix) Two sinusoidal voltages are given by  $e_1 = 10\sqrt{2}\sin(\omega t + \frac{\pi}{2})$  V and  $e_2 = 20\sqrt{2}\cos(\omega t)$  V, the ratio of form factor of  $e_1$  to  $e_2$  is

- (a) 2 (b) 1.11 (c) 1 (d) 0.5

x) The voltage in a circuit is given as  $v = 100 \sin \omega t$  V. If the frequency is 50 Hz, how long will it take for the voltage to rise to 50 V?

- (a) 20 mS (b) 10 mS (c) 3.33 mS (d) 1.66 mS

[2]

CO1

App

[2]

CO1

Apply

[2]

CO1

Apply

[2]

CO1

Apply

[2]

CO2

Apply

[2]

CO2

Apply

xi) The average values of two sinusoidal currents are $I_{1avg} = \frac{10}{\pi}$ A and $I_{2avg} = \frac{20}{\pi}$ A, then the ratio rms value of $I_2$ to $I_1$ is (a) 1 (b) 2 (c) 0.5 (d) cannot be determined	[2]	CO2	Underst and
xii) The instantaneous voltage is given by $v = 200\sqrt{2}\sin\left(\omega t - \frac{\pi}{2}\right)$ V with frequency 50 Hz. The voltage at $(1/6)^{th}$ cycle is given by ____ V. (a) 200 (b) -141.42 (c) 141.42 (d) -200	[2]	CO2	Apply
xiii) The voltage and current in a circuit are given as $V = 230\angle 30^\circ$ V and $I = 2\angle 15^\circ$ A. If the circuit works at 50 Hz, the power factor of the circuit will be (a) 0.866 lead (b) 0.965 lag (c) 0.707 lag (d) 0.707 lead	[2]	CO2	Apply
xiv) The instantaneous currents are given by $i_1 = 10\sqrt{2}\sin\left(100\pi t - \frac{\pi}{2}\right)$ A and $i_2 = 20\sqrt{2}\sin\left(120\pi t - \frac{\pi}{6}\right)$ A. The ratio of time period of current $i_1$ to the time period of current $i_2$ is (a) 5/6 (b) 6/5 (c) 1.11 (d) 1	[2]	CO2	Apply
xv) The rms value of voltage is $\frac{400}{\sqrt{2}}$ V and instantaneous voltage at $t = 0$ is 400 V. Then equation of voltage is given by (a) $v = 400\sin(\omega t)$ (b) $v = 400\sin\left(\omega t - \frac{\pi}{2}\right)$ (c) $v = 400\sin\left(\omega t + \frac{\pi}{2}\right)$ (d) $v = 400\sqrt{2}\sin\left(\omega t + \frac{\pi}{2}\right)$	[2]	CO2	Apply
Q2			
<b>Solve any three out of four</b>			
a) Draw the hysteresis loop of a ferromagnetic material and show residual magnetic flux density and coercive force in it. State the losses taking place in magnetic core of a transformer.	[5]	CO3	Underst and
b) Derive the emf equation of a single phase transformer. Also state the properties of an ideal transformer.	[5]	CO3	Underst and
c) A 25 kVA single phase transformer working at full load unity power factor has an efficiency of 94 %. The same efficiency is maintained when the transformer works at half load and 0.9 power factor. Determine the iron loss and full load copper loss.	[5]	CO3	Apply
d) In a 50 kVA, 1100V/220V single phase transformer, the iron and copper losses at full load are 350 W and 425 W respectively. Calculate the efficiency at (i) Full load with unity power factor (ii) Half load with unity power factor	[5]	CO3	Apply

Q.3	<p><b>Solve any three out of four</b></p> <p>a) Prove that a 3- phase, delta connected load consumes three times as much power as consumed by a star connected load.</p> <p>b) The electrical installation in a house is utilized as mentioned below:  i) 5 Tube lights, 18 W each, for 10 hrs. a day  ii) 6 ceiling fans, 60 W each, for 8 hrs. a day  iii) 1 electric oven of 1.2 KW for 30 minutes a day  iv) 2 electric geysers, 1.5 KW each for 1 hr a day.  Calculate the total cost of energy at the rate of Rs.7 per unit for 30 days.</p> <p>c) What is energy conservation? Suggest suitable measures for energy conservation in the house described in the above Q.3 b).</p> <p>d) A balanced 3-phase star connected load of 150 kW takes a leading current of 100 A with a line voltage of 1100 V, 50 Hz. Find the per phase values of the circuit elements of the load.</p>	[5]	CO4	Apply
		[5]	CO4	Apply
		[5]	CO4	Underst and
		[5]	CO4	Apply