

Total No. of Questions – [4]

Total No. of Printed Pages: [2]



PRN. No. 

PAPER CODE

U114-303A (Backlog)

**DECEMBER 2024 (Backlog) EXAM Sem-I****F.Y. B. Tech. (Common)****(PATTERN 2020)****COURSE NAME: Basic Electrical Engineering****COURSE CODE: ET10203A****Time: [2 Hrs.]****[Max. Marks: 60]****(\*) Instructions to candidates:**

- 1) Use of scientific calculator is allowed
- 2) Use suitable data where ever required
- 3) All questions are compulsory. Solve any **THREE** sub questions from **EACH** question

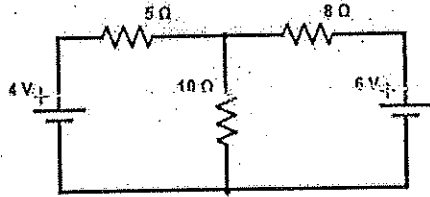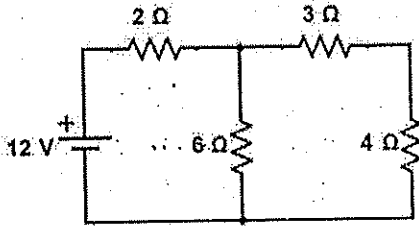Que. No.	Question Description	Max. Marks	CO mapped	BT Level
<b>Q1.</b>	<b>Solve any three sub questions from the following</b>			
	<p>A) Calculate the current in <math>10\ \Omega</math> in the circuit as shown in figure 1 using Norton's theorem.</p>  <p style="text-align: center;">Figure 1</p>	[5]	CO1	Apply
	<p>B) Find the voltage drop across <math>4\ \Omega</math> resistance in the circuit as shown in figure 2 using Thevenin's theorem.</p>  <p style="text-align: center;">Figure 2</p>	[5]	CO1	Apply
	C) Calculate power consumed by $4\ \Omega$ resistance in the circuit as shown in figure 2 using Norton's theorem.	[5]	CO1	Apply
	D) State and explain Kirchhoff's Current law (KCL) and Kirchhoff's voltage law (KVL) along with sign conventions used.	[5]	CO1	Understand

<b>Q2.</b>	<b>Solve any three sub questions from the following</b>			
	A) A resistance of $20\ \Omega$ , inductance of $0.2\ \text{H}$ and capacitance of $150\ \mu\text{F}$ are connected in series and are fed by a $230\text{V}$ , $50\text{Hz}$ single-phase ac supply. Find: i) inductive and capacitive reactance ii) impedance and admittance of circuit and iii) power factor of circuit.	[5]	CO2	Apply
	B) A series RLC circuit undergoing resonance has $R=5\ \Omega$ , $L=0.2\ \text{H}$ and $C=50\ \mu\text{F}$ . The applied voltage to circuit is $200\ \text{V}$ . Calculate: - i) resonant frequency ii) current at resonance and iii) voltage across inductance at resonance.	[5]	CO2	Apply
	C) A circuit consists of resistance of $4\ \Omega$ , inductance of $0.5\ \text{H}$ and a variable capacitance in series across $100\text{V}$ , $50\text{Hz}$ supply. Calculate: i) the value of capacitance to produce resonance ii) current flowing through the circuit and iii) voltage across capacitance at resonance.	[5]	CO2	Apply
	D) Derive an expression for current drawn and the average power consumed by a circuit consisting of a pure capacitor of capacitance ' $C$ ' connected across an ac source of $v = V_m \sin \omega t$ .	[5]	CO2	Under stand
<b>Q3.</b>	<b>Solve any three sub questions from the following</b>			
	A) At full-load, the copper and iron losses in a $100\ \text{kVA}$ transformer are each equal to $2.5\ \text{kW}$ . Find the efficiency at a load of $65\ \text{kVA}$ , power factor $0.8$ .	[5]	CO3	Apply
	B) A $40\ \text{kVA}$ , $6600\text{V}/230\text{V}$ , $50\ \text{Hz}$ , single-phase transformer has 30 turns on its secondary winding. Calculate the number of turns of the primary winding. Also calculate the primary and secondary winding full load currents.	[5]	CO3	Apply
	C) A $55\ \text{kVA}$ , $50\ \text{Hz}$ single- phase transformer has primary winding of 460 turns and secondary winding of 160 turns. The input side of the transformer is supplied with $2500\ \text{V}$ . Calculate: i) Secondary voltage ii) primary and secondary full load current and iii) maximum flux in the core.	[5]	CO3	Apply
	D) A $45\ \text{kVA}$ , $6000/200\ \text{V}$ , single- phase transformer has primary and secondary resistance of $8\ \Omega$ and $0.01\ \Omega$ respectively. The leakage reactance referred to primary side is $30\ \Omega$ . Determine the percentage voltage regulation at full-load, $0.6$ power factor lagging.	[5]	CO3	Apply
<b>Q4.</b>	<b>Solve any three sub questions from the following</b>			
	A) Draw a neat phasor diagram for a three-phase balanced star-connected resistive load in each phase across a symmetrical three-phase ac supply and hence derive the relationship between the line current and phase current. Also write relation between line voltage and phase voltage.	[5]	CO4	Apply
	B) Calculate the phase and line currents in a balanced delta- connected load taking $75\ \text{kW}$ at a power factor of $0.8$ lagging from a 3-phase, $440\ \text{V}$ supply. Also calculate the total reactive power in the circuit.	[5]	CO4	Apply
	C) A $440\text{-V}$ , DC motor is used to drive an irrigation pump. The efficiency of the motor is $85\%$ and that of the pump is $66\%$ . The pump is required to lift $240$ kilo- litres of water per hour to a height of $30$ meters. Calculate the current taken by the motor. Take ' $g$ ' as $9.81\ \text{m/s}^2$ . Assume $1\ \text{litre} = 1\ \text{kg}$ of water.	[5]	CO4	Apply
	D) An electric motor is driving a train weighing $100$ thousand kilograms upon an inclined track of $1$ in $100$ at a speed of $60\ \text{km/ hour}$ . The tractive resistance is $10\ \text{kg}$ per $1000\ \text{kg}$ of its weight. If the motor operates on $11\ \text{kV}$ , find the current taken by the motor assuming the overall efficiency of the system as $70\%$ . Take gravitational acceleration ' $g$ ' as $9.81\ \text{m/s}^2$ .	[5]	CO4	Apply