

Total No. of Questions – [2]

Total No. of Printed Pages: 1

G.R. No.	
----------	--

PAPER CODE	V124-395
------------	----------

March 2024 (INSEM) EXAM
F.Y.B. TECH. (E&TC) (SEMESTER - II)
COURSE NAME: Digital Electronics
COURSE CODE: ET12235
(PATTERN 2023)

Time: [40 min]

[Max. Marks: 20]

(*) Instructions to candidates:

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data wherever required
- 4) Solve any two sub questions from Question 1 and 2

Question No.	Question Description	Marks	CO mapped	Blooms Taxonomy Level
Q.1	a) Convert following numbers in decimal i) 54_{16} ii) 145_8 iii) $(10011001)_2$	[5]	1	Understand
	Perform Subtraction of following using 2's complement method 56 and 27		1	Apply
	b) Simplify the following Boolean expressions using the Boolean algebra rules and theorems. i) $[AB(C + BD + \overline{AB})]C$	[5]		
	c) Realize 1-bit full subtractor circuits using K-map. (use Logic gates only)	[5]	1	Apply
Q2	a) Design a 5-bit comparator using a single 7485 IC and one gate	[5]	2	Design
	b) Design a 16:1 mux using two 8:1 Mux Implement following using 8:1 Mux $f(A, B, C) = \sum m(0, 2, 3, 5, 6)$	[5]	2	Design
	c) Design a logic circuit for 4-bit Gray code to binary code conversion.	[5]	2	Design

