

PRN No.	
---------	--

PAPER CODE	U124-395
---------------	----------

May 2024 (ENDSEM) EXAM

F.Y.B. TECH. (SEMESTER - II)

COURSE NAME: Digital Electronics

Branch: E&TC

COURSE CODE:

ET12235

(PATTERN 2023)

Time: [1Hr. 30 Min]

[Max. Marks: 40]

(*) Instructions to candidates:

- 1) Figures to the right indicate full marks.
- 2) Use of scientific calculator is allowed
- 3) Use suitable data wherever required
- 4) All questions are compulsory. Solve any one sub question from each Question 1 and 2 and any three sub questions each from Questions 3 and 4.

Q. No.	Question Description	Max. Marks	CO mapped	BT Level
Q.1	a) i. Convert the given Gray code number to equivalent binary 001001011110010 ii. Consider a function 'F'. Show that $F.F'=0$ and $F+F'=1$	[5] [5]	CO1	Understand
	b) Minimize the following function using K-map $F(P, Q, R, S) = \sum m(4, 5, 6, 7, 8, 12) + d(1, 2, 3, 9, 11, 14)$		CO1	Understand
Q2	a) Design a combinational circuit with the three inputs and one output. the output is equal to logic-1 when the binary value of the input is less than 4 otherwise the output is logic-0	[5] [5]	CO2	Apply
	b) Implement the given logic function using a 4 : 1 multiplexer. $f(A,B,C) = \sum m(0, 2, 4, 6)$.		CO2	Apply
Q.3	a) Convert D flip flop into JK flip flop.	[5]	CO3	Apply
	b) Design and implement 3-bit synchronous counter using T flip flop.	[5]	CO3	Apply
	c) Design the sequential circuit for the given state diagram using T flip flop.	[5]	CO3	Apply

	<p>d) Design and implement circuit using D flip flop to detect the binary sequence 110.</p>	[5]	CO3	Analyze
Q.4	<p>a) Elaborate different Modeling styles used in VHDL.</p> <p>b) Write a VHDL code to design 1-bit full subtractor using dataflow modeling.</p> <p>c) Write a VHDL to implement a 2:1 multiplexer using structural style of model</p> <p>d) Design a 3 bit ALU which can perform any 4 logical operations and 4 arithmetic operations.</p>	<p>[5]</p> <p>[5]</p> <p>[5]</p> <p>[5]</p>	<p>CO4</p> <p>CO4</p> <p>CO4</p> <p>CO4</p>	<p>Understand</p> <p>Apply</p> <p>Apply</p> <p>Apply</p>